 




CIRCUITO DETECTOR DE PARIDAD CONFIGURABLE.

Usaremos el siguiente esquema tentativo



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity problema3_paridad is
    generic (n: positive);
    Port (entrada: in std_logic_vector ((n-1) downto 0);
          pi:in bit;
          z:out bit);
end problema3_paridad;
architecture Behavioral of problema3_paridad is
begin
    process (entrada,pi)
        variable cuenta,residuo: integer :=0;
    begin
        pasol:      for i in 0 to n-1 loop
                    if entrada(i)='1' then
                        cuenta:=cuenta+1;
                    end if;
                end loop pasol;
        --para chequear si es par o impar
        residuo:=cuenta mod 2;
        if pi='1' then
            if residuo=0 then z<='1';
            else z<='0';
            end if;
        else
            if residuo=0 then z<='0';
            else z<='1';
            end if;
        end if;
    end process;
end architecture;
```

```
        end if;
end process;
end Behavioral;
```

Para probar esto creamos el siguiente archivo de prueba

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity test_problema3 is
    Port ( pi : in bit;
          z : out bit;
          ent : in std_logic_vector(15 downto 0));
end test_problema3;

architecture Behavioral of test_problema3 is
    component problema3_paridad is
        generic (n: positive);
        Port (entrada :in std_logic_vector ((n-1) downto 0);
              pi:in bit;
              z:out bit);
    end component;

begin
    U: problema3_paridad generic map (15) port map (ent,pi,z);

end Behavioral;
```