

## **INFORME FINAL LAB1**

**"Síntesis y simulación de circuitos combinacionales con VHDL utilizando las herramientas de XILINX"**

5.- Se tiene un circuito con 4 entradas: SABELOTODO, DISEÑADOR, FALLA y ESTUDIOS, escriba un '1' a la salida del circuito para:

Diseñadores con éxito que nunca estudiaron  
Sabelotodos que estudiaban todo el tiempo.

a. Utilizando ACS Condicional:

```
Preg5a.vdl
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity preguntas is
    Port ( Sabelotodo : in std_logic;
          Diseñador : in std_logic;
          Falla : in std_logic;
          Estudios : in std_logic;
          Salida : out std_logic);
end preguntas;

architecture ASC_COND of preguntas is
    signal P,Q:std_logic;
begin
    P <='1' when(Diseñador and (not Falla) and (not Estudios))='1' else '0';
    Q <='1' when(Sabelotodo and Estudios)='1' else '0';
    Salida <= P or Q;
end ASC_COND;
```

```
CAD-SELECTIVO
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```


```
entity preguntas is
    Port ( Sabelotodo : in std_logic;
          Diseñador : in std_logic;
          Falla : in std_logic;
          Estudios : in std_logic;
          Salida : out std_logic);
end preguntas;
```

b) Utilizando ACS Selectivo

```
architecture ASC_SELECT of preguntas is
    signal T: std_logic_vector(1 downto 0);
begin
    T(1)<='1' when(Diseñador and (not Falla) and (not Estudios))='1' else '0';
    T(0)<='1' when(Sabelotodo and Estudios)='1' else '0';
with T select    Salida <= '0' when "00",
                '1' when others;
end ASC_SELECT;
```

## Informe Final Laboratorio 1 :Diseño Digital

 6.- Diseñe un Circuito sumador completo de 2 bits c/u



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Preg6 is
    Port ( a : in std_logic_vector(1 downto 0);--entradas a de 2 bits
          b : in std_logic_vector(1 downto 0);--entradas b de 2 bits
          cin : in std_logic;--Carry entrada
          cout : out std_logic;--Carry salida
          sum : out std_logic_vector(1 downto 0));--salida sum de 2 bits
end Preg6;
```

```
architecture flujo of Preg6 is --Sum2bits
    signal temp,temp2: std_logic_vector(1 downto 0);--Sirve para las sumas parciales
begin
    temp2(0) <= (a(0) and b(0))xor cin; --carry 0
    temp(0) <= (a(0) xor b(0)) xor cin; --a(0)+b(0)+Cin
    temp(1) <= (a(1) xor b(1)) xor temp2(0); --a(1)+(b1)+temp2(0)
    temp2(1) <= (a(1) and b(1)) xor temp2(0); --carry 1
    sum <=temp;
    cout <=temp2(1);
end flujo;
```

7.-Escriba el programa en VHDL, para el siguiente circuito:

PREG7.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity Preg7 is --MUX2A1
    Port ( A : in std_logic;
          B : in std_logic;
          Sel : in std_logic;
          Z : out std_logic);
end Preg7;
```


```
architecture Flujo of MUX2A1 is
begin
    Z<=A When Sel ='0' ELSE B;
end Flujo;
```

## Informe Final Laboratorio 1 :Diseño Digital

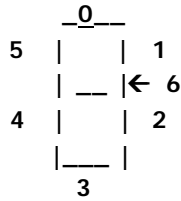8.- Escriba el programa en VHDL para un decodificador a 7 segmentos con una entrada de control.

PREG8.VHD

```
--DECODER HEX a 7 Segmentos
--  HEX:  in  STD_LOGIC_VECTOR (3 downto 0);
--  LED:  out  STD_LOGIC_VECTOR (6 downto 0);
--
-- segment encoding
```



```
--
--
--
--
--
--
--
library ieee;
use ieee.std_logic_1164.all;

entity Preg8 is
port(  control: in std_logic;
      bcd: in  std_logic_vector(3 downto 0);
      LED: out std_logic_vector(6 downto 0));
end Preg8;
    architecture flujo of Preg8 is
begin
    conv: process (bcd)
begin
if control='1' then
case bcd is
when "0000" => LED <= "0111111" ; --0
when "0001" => LED <= "0000110" ; --1
when "0010" => LED <= "1011011" ; --2
when "0011" => LED <= "1001111" ; --3
when "0100" => LED <= "1100110" ; --4
when "0101" => LED <= "1101101" ; --5
when "0110" => LED <= "1111101" ; --6
when "0111" => LED <= "0000111" ; --7
when "1000" => LED <= "1111111" ; --8
when "1001" => LED <= "1101111" ; --9
when "1010" => LED <= "1110111" ; --A
when "1011" => LED <= "1111100" ; --B
when "1100" => LED <= "0111001" ; --C
when "1101" => LED <= "1111001" ; --D
when "1110" => LED <= "1111001" ; --E
when others => LED <= "1110001" ; -- solo nos queda la F
end case;
else
case bcd is
when "0000" => LED <= "1000000"; --0
when "0001" => LED <= "1111001"; --1
when "0010" => LED <= "0100100"; --2
```

## Informe Final Laboratorio 1 :Diseño Digital

```
when "0011" => LED <= "0110000"; --3
when "0100" => LED <= "0011001"; --4
when "0101" => LED <= "0010010"; --5
when "0110" => LED <= "0000010"; --6
when "0111" => LED <= "1111000"; --7
when "1000" => LED <= "0000000"; --8
when "1001" => LED <= "0010000"; --9
when "1010" => LED <= "0001000"; --A
when "1011" => LED <= "0000011"; --B
when "1100" => LED <= "1000110"; --C
when "1101" => LED <= "0100001"; --D
when "1110" => LED <= "0000110"; --E
when others => LED <= "0001110"; --F
end case;
end if;
end process conv;
end flujo;
```

9. -Escriba el programa en VHDL para un circuito con las siguientes características:

Entradas: 4 → D3,D2,D1,D0 ..... Datos  
          2 → S1,S0 ..... Control  
Salidas: 4 → Q3,Q2,Q1,Q0 ..... Salida de Datos

Si:

S1,S0="00" → Q <= D  
S1,S0="01" → Q un bit a la izquierda.  
S1,S0="10" → Q un bit a la Derecha  
S1,S0="01" → Q no se altera.

Nota: Puede utilizar el símbolo &(concatenar).

PREG9.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Preg9 is
  Port ( D : in std_logic_vector(3 downto 0); --Entrada de datos (D3)(D2)(D1)(D0)
        S : in std_logic_vector(1 downto 0); --Control S0 S2
        Q : inout std_logic_vector(3 downto 0)); --Salida (Q3)(Q2)(Q1)(Q0)
end Preg9;

architecture ASC_SELECT of Preg9 is
begin
with S select Q <= D when "00",
              D(2)&D(1)&D(0)&D(3) when "01",
              D(0)&D(3)&D(2)&D(1) when "10",
              Q when others;

end ASC_SELECT;
```

## Informe Final Laboratorio 1 :Diseño Digital

### 10.- Indique las características del CPLD de Xilinx XC95108PC84 CPLD

#### XC95108 In-System Programmable

##### Características

- 7.5 ns de retardo logico pin a pin en todos sus pines
- fCNT a 125 MHz
- 108 macroceldas con 2400 compuertas usables
- Arriba de 108 pines de I/O
- 5 V entrada - sistema programable (ISP)
- aguante de 10,000 ciclos de programacion/borrado
- Programa/borra muy por encima del voltaje comercial y rango de temperatura
- Mejora su arquitectura cerrada
- Bloque de funciones flexible 36V18
- 90 condiciones del producto manejan cualquiera o todas las 18 macroceldas dentro del Bloque de la Función IEEE Extenso Std 1149.1 límite-examinan (JTAG) el apoyo
  - el modo de reducción de poder Programmable en cada macrocell
  - Slew el mando de la proporción en los rendimientos individuales
  - el Usuario de o la capacidad de alfiler de tierra programable
  - Extended que la seguridad del modelo ofrece para protección del plan
  - High-drive 24 rendimientos de MA
  - 3.3 V o 5 V la capacidad de I/O
  - Advanced CMOS 5V tecnología de FastFLASH
  - Supports la programación paralela de más de un XC9500 concurrentemente
  - Available en el 84-alfiler PLCC, 100-alfiler PQFP, 100-alfiler TQFP y 160-alfiler los paquetes de PQFP

##### Rangos Absolutos Maximos

Symbol	Parameter	Value	Units
V <sub>CC</sub>	Supply voltage relative to GND	-0.5 to 7.0	V
V <sub>IN</sub>	DC input voltage relative to GND	-0.5 to V <sub>CC</sub> + 0.5	V
V <sub>TS</sub>	Voltage applied to 3-state output with respect to GND	-0.5 to V <sub>CC</sub> + 0.5	V
T <sub>STG</sub>	Storage temperature	-65 to +150	°C
T <sub>SOL</sub>	Max soldering temperature (10 s @ 1/16 in = 1.5 mm)	+260	°C

#### DC Characteristics Over Recommended Operating Conditions

Symbol	Parameter	Test Conditions	Min	Max	Units
V <sub>OH</sub>	Output high voltage for 5 V operation	I <sub>OH</sub> = -4.0 mA V <sub>CC</sub> = Min	2.4		V
	Output high voltage for 3.3 V operation	I <sub>OH</sub> = -3.2 mA V <sub>CC</sub> = Min	2.4		V
V <sub>OL</sub>	Output low voltage for 5 V operation	I <sub>OL</sub> = 24 mA V <sub>CC</sub> = Min		0.5	V
	Output low voltage for 3.3 V operation	I <sub>OL</sub> = 10 mA V <sub>CC</sub> = Min		0.4	V
I <sub>IL</sub>	Input leakage current	V <sub>CC</sub> = Max V <sub>IN</sub> = GND or V <sub>CC</sub>		±10.0	µA
I <sub>IH</sub>	I/O high-Z leakage current	V <sub>CC</sub> = Max V <sub>IN</sub> = GND or V <sub>CC</sub>		±10.0	µA
C <sub>IN</sub>	I/O capacitance	V <sub>IN</sub> = GND f = 1.0 MHz		10.0	pF
I <sub>CC</sub>	Operating Supply Current (low power mode, active)	V <sub>I</sub> = GND, No load f = 1.0 MHz		100 (Typ)	ma

# Informe Final Laboratorio 1 :Diseño Digital


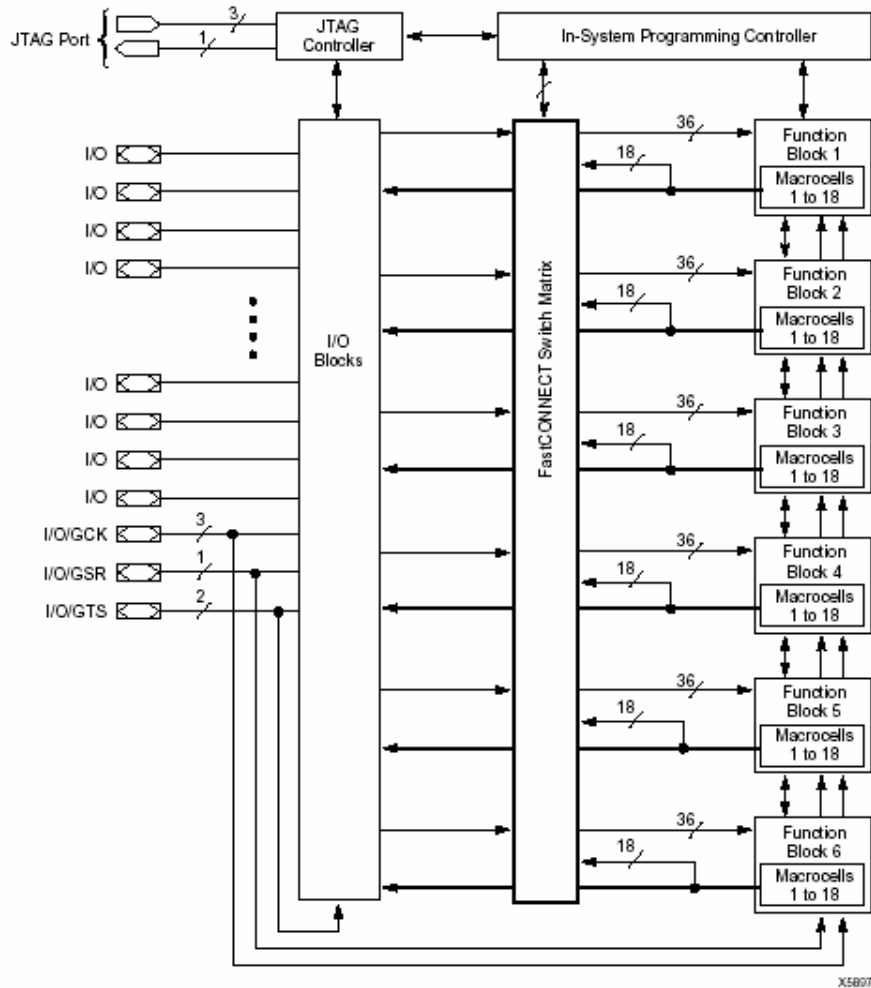


Figure 2: XC95108 Architecture

## Ordering Information

 

### Speed Options

- 20 20 ns pin-to-pin delay
- 15 15 ns pin-to-pin delay
- 10 10 ns pin-to-pin delay
- 7 7 ns pin-to-pin delay

### Packaging Options

- PC84 84-Pin Plastic Leaded Chip Carrier (PLCC)
- PQ100 100-Pin Plastic Quad Flat Pack (PQFP)
- TQ100 100-Pin Very Thin Quad Flat Pack (TQFP)
- PQ160 160-Pin Plastic Quad Flat Pack (PQFP)

### Temperature Options

- C Commercial 0°C to +70°C
- I Industrial -40°C to +85°C

## Informe Final Laboratorio 1 :Diseño Digital

### Component Availability

Pins		84	100		160
Type		Plastic PLCC	Plastic PQFP	Plastic TQFP	Plastic PQFP
Code		PC84	PQ100	TQ100	PQ160
XC95108	-20	C(I)	C(I)	C(I)	C(I)
	-15	C(I)	C(I)	C(I)	C(I)
	-10	C(I)	C(I)	C(I)	C(I)
	-7	C(I)	C(I)	C(I)	C(I)

C = Commercial = 0° to +70°C I = Industrial = -40° to +85°C