

Informe Final Laboratorio 4 :Diseño Digital

UNIVERSIDAD NACIONAL MAYOR DE SAN MARCOS FACULTAD DE INGENIERIA ELECTRONICA ESCUELA DE ELECTRONICA


1.-Diseñe un ckto full_ad der utilizando cualquier estilo de l VHDL.

FA.vhd :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity FA is
  Port ( Cin : in std_logic;
        A : in std_logic;
        B : in std_logic;
        S : out std_logic;
        Cout : out std_logic);
end FA;

 architecture Behavioral of FA is
begin
S<=A Xor B Xor Cin;
Cout<=(A and B) or (A and Cin) or(B and Cin);
end Behavioral;
```



2.- Desñe un sumador-restador de 8 bits utilizando sumadores de 2 bits(full-addder) utilice el estilo estructural.

Suma resta.vhd :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity sum_rest is
  Port ( Cin : in std_logic;
        A : in std_logic_vector(7 downto 0);
        B : in std_logic_vector(7 downto 0);
        S : out std_logic_vector(7 downto 0);
        Cout : out std_logic);
end sum_rest;


architecture Estructural of sum_rest is
  component fa
    Port ( Cin : in std_logic;
          A : in std_logic;
          B : in std_logic;
          S : out std_logic;
          Cout : out std_logic);
  end component;
  signal C,P:std_logic_vector(7 downto 0);
begin
P(0)<=Cin Xor B(0);
P(1)<=Cin Xor B(1);
P(2)<=Cin Xor B(2);
```

Informe Final Laboratorio 4 :Diseño Digital

```

P(3)<=Cin Xor B(3);
P(4)<=Cin Xor B(4);
P(5)<=Cin Xor B(5);
P(6)<=Cin Xor B(6);
P(7)<=Cin Xor B(7);
S_R00:fa port MAp(Cin,A(0),P(0),S(0),C(0));
suma_resta: For i in 0 to 6 Generate
    S_R:fa port map(C(i),A(i+1),P(i+1),S(i+1),C(i+1));
end generate;
    Cout<=C(7);
end Estructural;

```

 

3.-

Usa Suma,Suma2,Suma3,Suma4,Incr5:

Suma.vhd:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity suma is
    Port ( Cin : in std_logic;
          A : in std_logic;
          B : in std_logic;
          S : out std_logic_vector(1 downto 0));
end suma;

architecture Behavioral of suma is
    component fa
        Port ( Cin : in std_logic;
              A : in std_logic;
              B : in std_logic;
              S : out std_logic;
              Cout : out std_logic);
    end component;
begin
    sum_es:fa port map(Cin,A,B,S(0),S(1));
end Behavioral;

```



sumador2.vhd:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity sumador2 is
    Port ( Cin : in std_logic;
          A : in std_logic_vector(1 downto 0);
          B : in std_logic_vector(1 downto 0);
          S : out std_logic_vector(2 downto 0)
          );

```

Informe Final Laboratorio 4 :Diseño Digital

```

end sumador2;

architecture estructural of sumador2 is
  component fa
    Port ( Cin : in std_logic;
          A : in std_logic;
          B : in std_logic;
          S : out std_logic;
          Cout : out std_logic);
  end component;
  signal C:std_logic_vector(1 downto 0):="00";
begin
  suma1:fa port MAp(Cin,A(0),B(0),S(0),C(0));
  suma2:fa port MAp(C(0),A(1),B(1),S(1),S(2));
end estructural;

```



sumador3.vhd:


```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity sumador3 is
  Port ( Cin : in std_logic;
        A : in std_logic_vector(2 downto 0);
        B : in std_logic_vector(2 downto 0);
        S : out std_logic_vector(3 downto 0)
        );
end sumador3;

architecture estructural of sumador3 is
  component fa
    Port ( Cin : in std_logic;
          A : in std_logic;
          B : in std_logic;
          S : out std_logic;
          Cout : out std_logic);
  end component;
  signal C:std_logic_vector(2 downto 0):="000";
begin
  pri: fa port MAp(Cin,A(0),B(0),S(0),C(0));
  suma: For i in 0 to 1 Generate
    Sum:fa port map(C(i),A(i+1),B(i+1),S(i+1),C(i+1));
  end generate;
  S(3)<=C(2);
end estructural;

```

 

sumador4.vhd:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```


Informe Final Laboratorio 4 :Diseño Digital

```

entity sumador4 is
  Port ( Cin : in std_logic;
        A : in std_logic_vector(3 downto 0);
        B : in std_logic_vector(3 downto 0);
        S : out std_logic_vector(4 downto 0)
        );
end sumador4;

architecture estructural of sumador4 is
  component fa
    Port ( Cin : in std_logic;
          A : in std_logic;
          B : in std_logic;
          S : out std_logic;
          Cout : out std_logic);
  end component;
  signal C:std_logic_vector(3 downto 0):="0000";
begin
  pri: fa port Map(Cin,A(0),B(0),S(0),C(0));
  suma: For i in 0 to 2 Generate
    Sum:fa port map(C(i),A(i+1),B(i+1),S(i+1),C(i+1));
  end generate;
  S(4)<=C(3);
end estructural;

```

 

incr5.vhd:


```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity INCR5 is
  Port (Cin:in std_logic;
        Dato:in std_logic_vector(4 downto 0);
        Salida:out std_logic_vector(5 downto 0)
        );
end INCR5;

architecture Estructural of INCR5 is
  component fa
    Port ( Cin : in std_logic;
          A : in std_logic;
          B : in std_logic;
          S : out std_logic;
          Cout : out std_logic);
  end component;
  signal C:std_logic_vector(4 downto 0):="00000";
begin
  pri: fa port Map(Cin,dAto(0),'0',Salida(0),C(0));
  suma: For i in 0 to 3 Generate
    Sum:fa port map(C(i),dAto(i+1),'0',Salida(i+1),C(i+1));
  end generate;
  Salida(5)<=C(4);
end Estructural;

```

 

Informe Final Laboratorio 4 :Diseño Digital

Y el programa final es:

PREG3.VHD :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Preg3 is
    Port ( D : in std_logic_vector(31 downto 0);
          sum : out std_logic_vector(5 downto 0));
end Preg3;

architecture estructural of Preg3 is
    component suma
        Port ( Cin : in std_logic;
              A : in std_logic;
              B : in std_logic;
              S : out std_logic_vector(1 downto 0)
            );
    end component;
    component sumador2
        Port ( Cin : in std_logic;
              A : in std_logic_vector(1 downto 0);
              B : in std_logic_vector(1 downto 0);
              S : out std_logic_vector(2 downto 0)
            );
    end component;
    component sumador3
        Port ( Cin : in std_logic;
              A : in std_logic_vector(2 downto 0);
              B : in std_logic_vector(2 downto 0);
              S : out std_logic_vector(3 downto 0)
            );
    end component;
    component sumador4
        Port ( Cin : in std_logic;
              A : in std_logic_vector(3 downto 0);
              B : in std_logic_vector(3 downto 0);
              S : out std_logic_vector(4 downto 0)
            );
    end component;
    component incr5
        Port (Cin:in std_logic;
              Dato:in std_logic_vector(4 downto 0);
              Salida:out std_logic_vector(5 downto 0)
            );
    end component;
    signal S0,s1,s2,s3,s4,s5,s6,s7:std_logic_vector(1 downto 0):="00";
    signal s8,s9,s10,s11:std_logic_vector(2 downto 0):="000";
    signal s12,s13:std_logic_vector(3 downto 0):="0000";
    signal s14:std_logic_vector(4 downto 0):="00000";
    signal s15:std_logic_vector(5 downto 0):="000000";
begin
    D2y0: suma port MAp(D(2),D(1),D(0),S0);
    D5y3: suma port MAp(D(5),D(4),D(3),S1);
    D8y6: suma port MAp(D(8),D(7),D(6),S2);
    D11y9: suma port MAp(D(11),D(10),D(9),S3);
    D14y12: suma port MAp(D(14),D(13),D(12),S4);
    D17y15: suma port MAp(D(17),D(16),D(15),S5);
    D20y18: suma port MAp(D(20),D(19),D(18),S6);
    D23y21: suma port MAp(D(23),D(22),D(21),S7);
```

Informe Final Laboratorio 4 :Diseño Digital

```
DS01y24: sumador2 port MAp(D(24),S0,S1,s8);
DS23y25: sumador2 port MAp(D(25),S2,S3,s9);
DS45y26: sumador2 port MAp(D(26),S4,S5,s10);
DS57y27: sumador2 port MAp(D(27),S6,S7,s11);

DS8y9y28: sumador3 port MAp(D(28),S8,S9,s12);
DS10y11y29: sumador3 port MAp(D(29),S10,S11,s13);

DS12y13y30: sumador4 port MAp(D(30),S12,S13,s14);

DS14y31: incr5 port MAp(D(31),S14,S15);
sum<=S15;
end estructural;
```

h/d	00010001001110101010011110000001	1000010001111011001110110110100	0110011011001011100101111101010
sum	13	17	19

4:

Usa a **FDD.vhd** :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity FFD is
    Port ( CLK : in std_logic;
          D : in std_logic;
          Q : out std_logic);
end FFD;

architecture Behavioral of FFD is
begin
process (Clk)
begin
IF CLK='1' THEN Q<=d; END IF;
end process;
end Behavioral;
```

y **PREG4.VHD** :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity preg4 is
    Port ( clk : in std_logic;
          D : in std_logic_vector(15 downto 0);
          Q : OUT std_logic_vector(15 downto 0));
end preg4;

architecture Despll6bits of preg4 is
component FFD
    Port ( CLK : in std_logic;
          D : in std_logic;
          Q : out std_logic);
end component;
begin
registrol6: for i in 0 to 15 generate
par_par:FFD Port Map(Clk,D(i),Q(i));
end generate registrol6;
end Despll6bits;
```

Informe Final Laboratorio 4 :Diseño Digital

/clk												
h/d	48772	56124	19912	52220	20718	5362	37277	32453	54910	53534	59449	54436
h/q	X	56124	52220	5362	32453	53534	54436					

5.- Crear una entidad y arquitectura donde el usuario tenga la capacidad de generar un registro de "n" bits.

A nuestro archivo lo llamaremos registro.vhd :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity registro is
generic(numero:positive);
Port ( clk : in std_logic;
      D : in std_logic_vector((numero-1) downto 0);
      Q : out std_logic_vector((numero-1) downto 0));
end registro;
```

```
architecture Behavioral of registro is
component FFD
Port ( CLK : in std_logic;
      D : in std_logic;
      Q : out std_logic);
end component;
begin
registros: for i in 0 to numero-1 generate
par_par:FFD Port Map(Clk,D(i),Q(i));
end generate registros;
end Behavioral;
```

y este funciona con el archivo anterior **FFD.vhd**

Y para probar su funcionamiento, crearemos un registro de 10 bits.

Y lo llamaremos registro10.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity registro10 is
Port ( clk : in std_logic;
      D : in std_logic_vector(10 downto 0);
      Q : out std_logic_vector(10 downto 0));
end registro10;

architecture estructural of registro10 is
component registro
generic(numero:positive);
Port ( clk : in std_logic;
      D : in std_logic_vector((numero-1) downto 0);
      Q : out std_logic_vector((numero-1) downto 0));
end component;
```

Informe Final Laboratorio 4 :Diseño Digital

```
end component;  
begin  
regis:registro generic map(10) Port MAP(clk,D,Q);  
end estructural;
```

Su simulacion es:

6:

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;  
  
entity preg6 is  
  Port ( C : in bit;  
        D : in std_logic_vector(7 Downto 0);  
        P : out std_logic);  
end preg6;  
  
architecture Estructural of preg6 is  
  
begin  
  process(D)  
    variable num_bits : integer;  
    variable paridad: integer;  
  begin  
    num_bits:=0;  
    for i in 0 to 7 loop  
      if D(i) ='1' then  
        num_bits := num_bits +1;  
      end if;  
    end loop;  
    paridad:=(num_bits mod 2);  
    case C is  
      when '1' =>if paridad=0 then P<='0'; else p<='1'; end if;  
      when '0' =>if paridad=0 then P<='1'; else p<='0'; end if;  
    end case;  
  end process;  
end Estructural;
```

